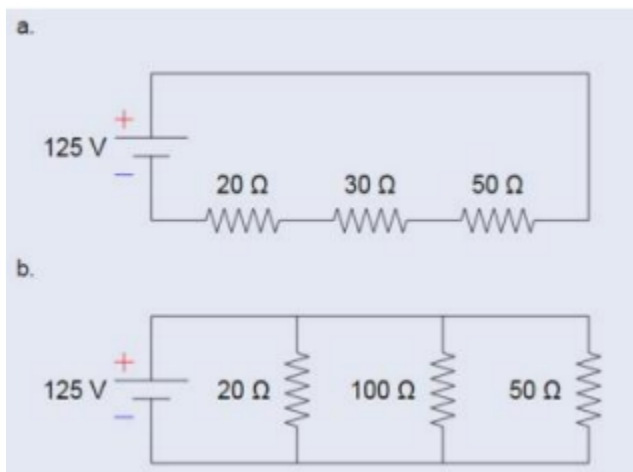


Embedded Systems & IoT April -July 2026 Lab Exercise: Schematics with ESP32

Wambati, Sylvia Wavinya
159819
ICS 4E

Part A



For each of these circuits:

1. Calculate the total resistance in ohms,

A. Total Resistance = $R_1 + R_2 + R_3$

$$20 + 30 + 50 = 100\Omega$$

B. Total Resistance = $1/R_1 + 1/R_2 + 1/R_3$

$$1/20 + 1/100 + 1/50 = 0.08$$

$$1/0.08 = 12.5\Omega$$

2. Calculate the total current from the power supply

A. $I = V/R$

$$I = 125/100 = 1.25A$$

B. $I = V/R$

$$125/12.5 = 10A$$

3. Calculate the current through each resistor

A. $I_1 = I_2 = I_3 = \text{Total current} = 1.25A$

B. $I_1 = 125/20 = 6.25A$

$$I_2 = 125/100 = 1.25A$$

$$I_3 = 125/50 = 2.5A$$

4. Calculate the Voltage drop through each resistor

A. $V=IR$

$$V1 = 1.25 * 20 = 25V$$

$$V2 = 1.25 * 30 = 37.5V$$

$$V3 = 1.25 * 50 = 62.5v$$

B. $V1=V2=V3=Total\ Voltage= 125V$

5. Calculate the Power dissipated through each resistor (use Watt's Law: Power = Voltage * Current)

A. $P=VI$

$$P1 = 25 * 1.25 = 31.25W$$

$$P2 = 37.5 * 1.25 = 46.875W$$

$$P3 = 62.5 * 1.25 = 78.128W$$

B. $P=VI$

$$P1 = 125 * 6.25 = 781.25W$$

$$P2 = 125 * 1.25 = 156.25W$$

$$P3 = 125 * 2.5 = 312.5W$$